
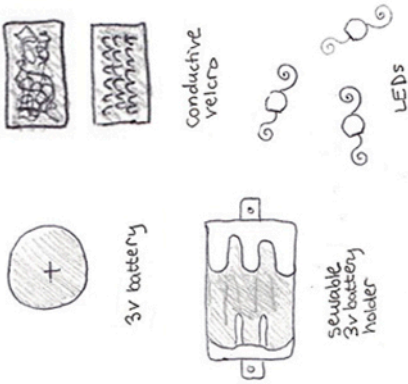


LED BRACELET WITH CONDUCTIVE VELCRO SWITCH

COMPONENTS

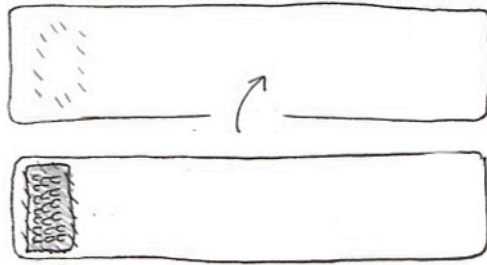

STEP 1




stitch conductive velcro in place with regular thread and turn felt over

STEP 2




stitch the second piece of velcro in place

STEP 3

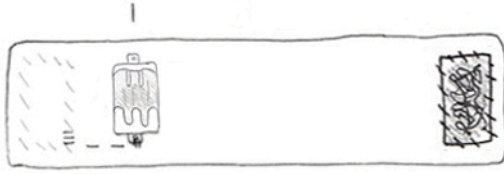


stitch from velcro to battery holder with conductive thread.

STEP 4

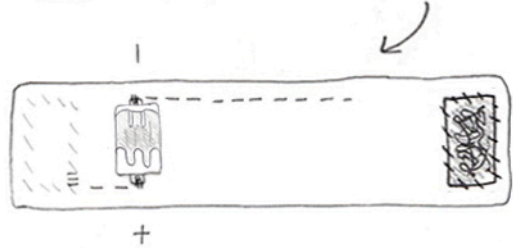


with a new piece of conductive thread stitch from the other side of the battery holder. stop before reaching the velcro. End stitch.

STEP 5

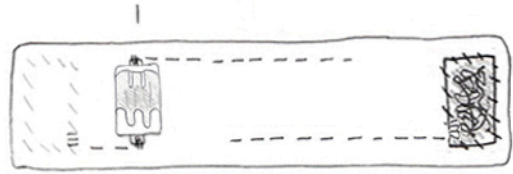


with a new piece of conductive thread stitch from velcro. stop before reaching the battery. End stitch.

STEP 6

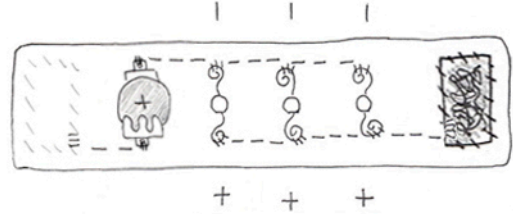

stitch LEDs in place finally, add 3V battery

COMPLETED CIRCUIT

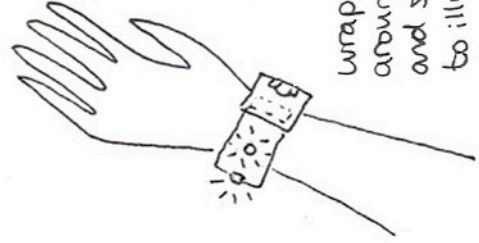

wrap bracelet around wrist and secure velcro to illuminate the LEDs